



Ministry of Higher Education and  
Scientific Research  
Tikrit University  
Engineering Collage – Al shirqat  
**FUNDAMENTALS OF  
ELECTRICAL ENGINEERING**  
**LECTURE 9**



## **MAXIMUM POWER TRANSFER THEOREM**

PREPARED BY  
TEACHING ASSISTANT

الصباحي Classroom: xtofyek4

المسائي Classroom: cftcvpvp

**ABDULLAH AHMED ALWAN**



# General Objectives:

## ➤ **Understanding the Scientific Basis of the Theory:**

- Defining the theory and its basic concept
- Clarifying its practical applications in electrical and electronic systems

## ➤ **Achieving High Efficiency in Energy Use:**

- Ensuring the maximum transfer of energy from the source to the load
- Improving the performance of electrical and electronic systems based on the principles of the theory

## ➤ **Enhancing Analytical Thinking and Engineering Skills:**

- Using mathematical models to explain the operation of electrical systems
- Analyzing electrical circuits to achieve the optimal state for energy transfer.



# Specific objectives:

## ➤ **Mastering the Theoretical Conditions:**

- Understanding that maximum power transfer occurs when the load resistance equals the internal resistance of the source.
- Recognizing the cases where the theory applies and where it does not.

## ➤ **Practical Application of the Theory:**

- Calculating the maximum power that can be transferred from the source to the load in various electrical circuits.

## ➤ **Training in Circuit Design:**

- Designing electrical circuits that meet the conditions of the theory.
- Selecting load and source components to achieve optimal efficiency.

## ➤ **Linking Theory to Practical Applications:**

- Understanding the theory's applications in electrical devices (such as communication and power systems).
- Analyzing and improving system efficiency in renewable energy applications.



# Introduction

➤ **Maximum Power Transfer Theorem:** The Maximum Power Transfer Theorem is one of the most important theories in electrical circuit analysis. It addresses how to transfer the maximum possible amount of electrical power from a power source to a specific load.

## ➤ **Theory Concept:**

The theorem states that the maximum power transfer from a power source to a load occurs when the load resistance  $R_L$  is exactly equal to the internal resistance of the source  $R_S$ , or the equivalent resistance of the source if it consists of multiple resistances.

## ➤ **Practical Applications:**

- Designing communication systems to effectively transmit signals.
- Improving the efficiency of power transfer in electrical power systems.
- Designing electronic circuits to ensure devices operate at optimal efficiency.



# Thevenin's Theorem

## Solution method:

### 1. Calculating the Source's Equivalent Resistance:

- If you have a complex circuit containing a voltage source and other components (resistors, current sources), start by calculating the source's equivalent resistance. Follow these steps:
- **Eliminate the effect of voltage sources:** Replace internal voltage sources with a short circuit.
- **Eliminate the effect of current sources:** Replace internal current sources with an open circuit.
- **Calculate the equivalent resistance** between the points where the load will be connected.



# Thevenin's Theorem

## Solution method:

### 2. Matching the Resistance Between Source and Load:

Make the load resistance ( $R_L$ ) equal to the source's equivalent resistance ( $R_{Th}$ ). This adjustment ensures maximum power is transferred from the source to the load.

### 3. Calculating the Transferred Power:

The power transferred to the load can be calculated using the following equation:

$$P_{max} = \frac{v_{Th}^2}{4R_{Th}}$$

Where:

$v_{Th}$ : Thevenin equivalent voltage.

$4R_{Th}$ : Thevenin equivalent resistance



# Maximum Power Transfer Theorem

**Maximum power is transferred** to the load when the load resistance equals the Thevenin resistance as seen from the load ( $R_L = R_{Th}$ ).

➤ For maximum power transfer  $\Rightarrow \mathbf{R_L = R_{Th}}$

$$i = \frac{v_{Th}}{R_L + R_{Th}}$$

$$P = i^2 R_L = \left( \frac{v_{Th}}{R_L + R_{Th}} \right)^2 \cdot R_L$$

At maximum power transfer  $\Rightarrow \mathbf{R_L = R_{Th}}$

$$P_{max} = \left( \frac{v_{Th}}{R_{Th} + R_{Th}} \right)^2 \cdot R_{Th} = \left( \frac{v_{Th}}{2R_{Th}} \right)^2 \cdot R_{Th}$$

$$P_{max} = \frac{v_{Th}^2}{4R_{Th}}$$

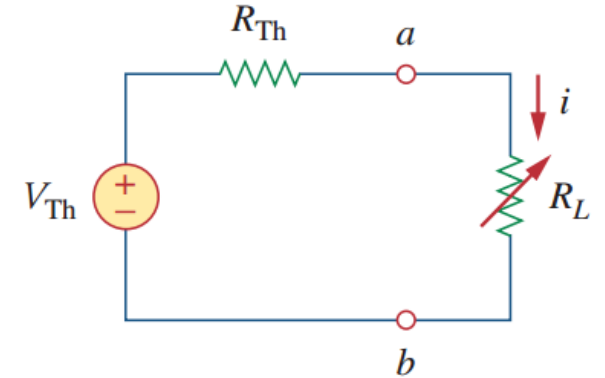


Figure 9-1 The circuit used for maximum power transfer.

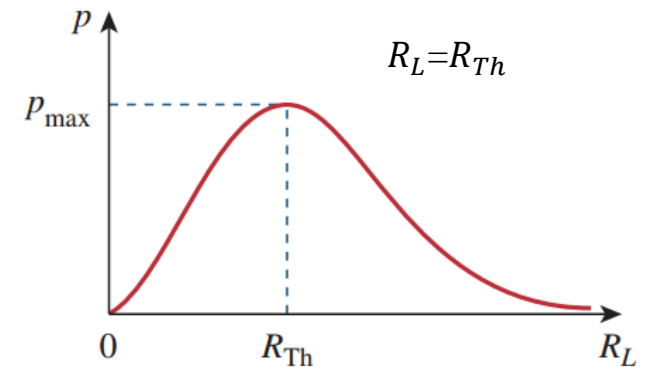


Figure 9-2 Power delivered to the load as a function of  $R_L$



# Maximum Power Transfer Theorem

$$P_{max} = \left( \frac{v_{Th}}{R_L + R_{Th}} \right)^2 \times R_L = \frac{(v_{Th})^2}{(R_L + R_{Th})^2} \times R_L$$

$$\frac{dP_L}{dR_L} = 0$$

$$\frac{dP_L}{dR_L} = V_{th}^2 \frac{(R_{th} + R_L)^2 - 2R_L(R_{th} + R_L)}{(R_{th} + R_L)^4}$$

$$(R_{th} + R_L)^2 - 2R_L(R_{th} + R_L) = 0$$

$$R_{th}^2 + 2R_{th}R_L + R_L^2 - 2R_LR_{th} - 2R_L^2 = 0$$

$$R_{th}^2 - R_L^2 = 0$$

$$R_{th}^2 = R_L^2 \implies \boxed{R_{th} = R_L}$$


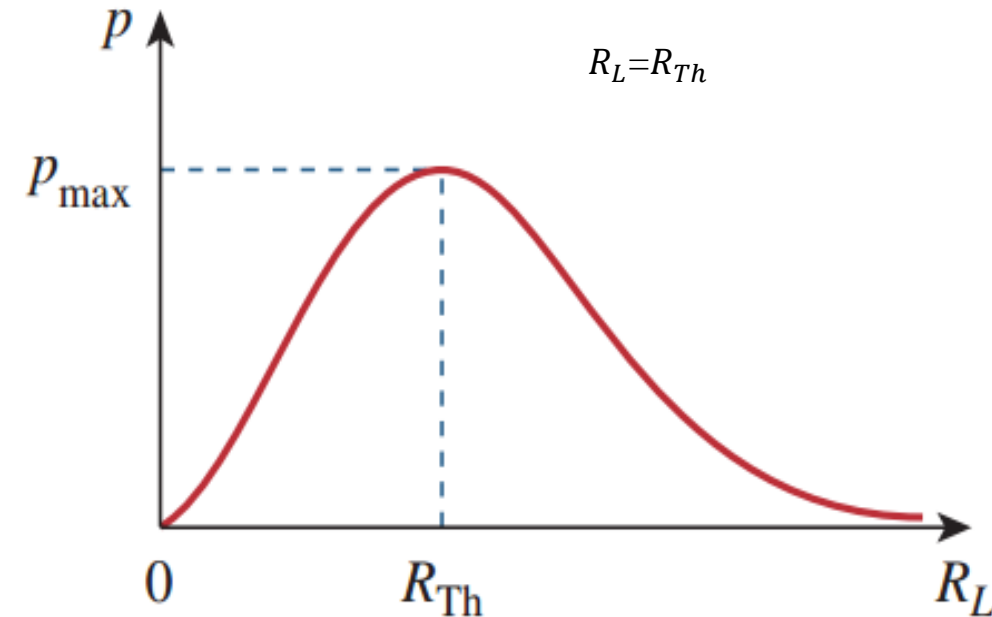


Figure 9-2 Power delivered to the load as a function of  $R_L$

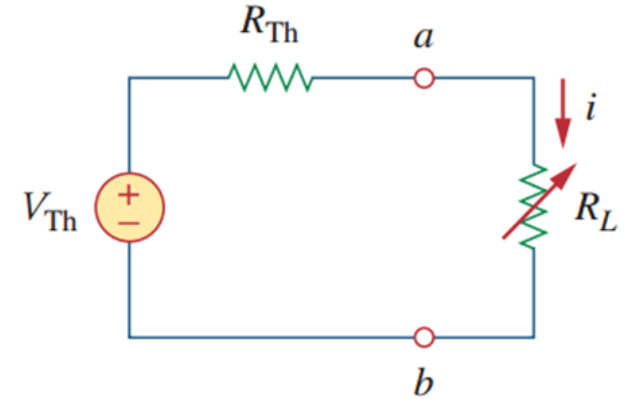

# Maximum Power Transfer Theorem

**Example 1:** For the circuit below, determine the value of  $R$  for maximum power to  $R$ , and calculate the power delivered under these conditions.




**Solution:**

$$R_{Th} = R_3 + R_1 \parallel R_2 = 8 \, \Omega + \frac{(6 \, \Omega)(3 \, \Omega)}{6 \, \Omega + 3 \, \Omega} = 8 \, \Omega + 2 \, \Omega$$

$$R = R_{Th} = \mathbf{10 \, \Omega}$$

$$E_{Th} = \frac{R_2 E}{R_2 + R_1} = \frac{(3 \, \Omega)(12 \, \text{V})}{3 \, \Omega + 6 \, \Omega} = \frac{36 \, \text{V}}{9} = \mathbf{4 \, \text{V}}$$
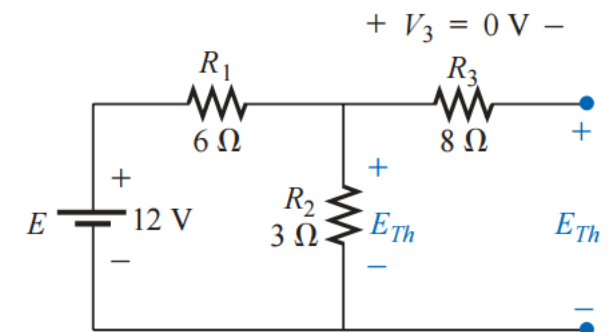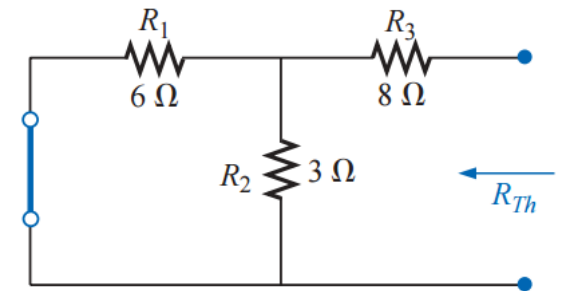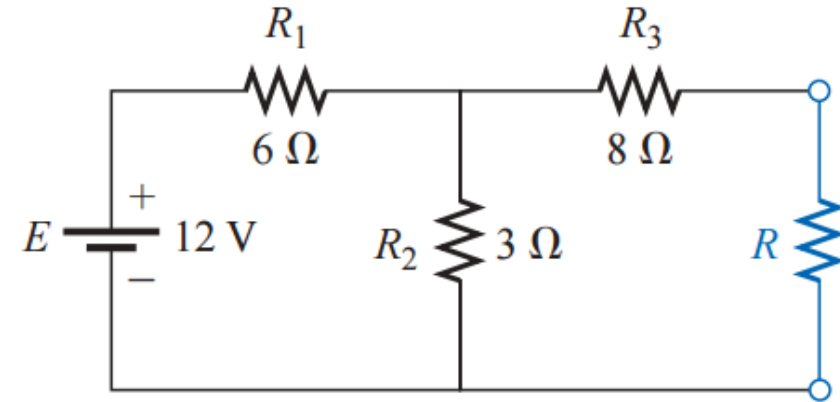
$$P_{L_{\max}} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(4 \, \text{V})^2}{4(10 \, \Omega)} = \mathbf{0.4 \, \text{W}}$$







# Maximum Power Transfer Theorem

**Example 2:** Find the value of  $R_L$  in the figure below for maximum power to  $R_L$ , and determine the maximum power

**Solution:**

$$R_{Th} = R_1 + R_2 + R_3 = 3\ \Omega + 10\ \Omega + 2\ \Omega = 15\ \Omega$$

$$R_L = R_{Th} = \mathbf{15\ \Omega}$$

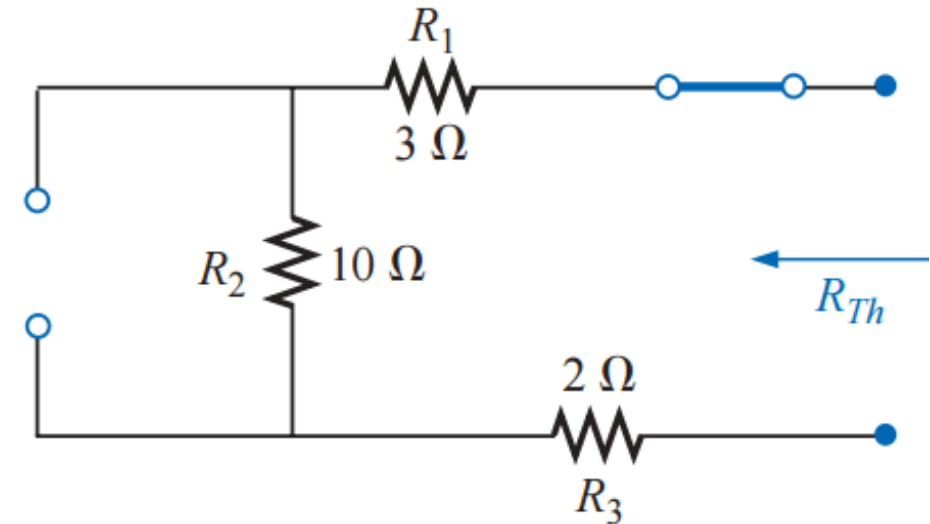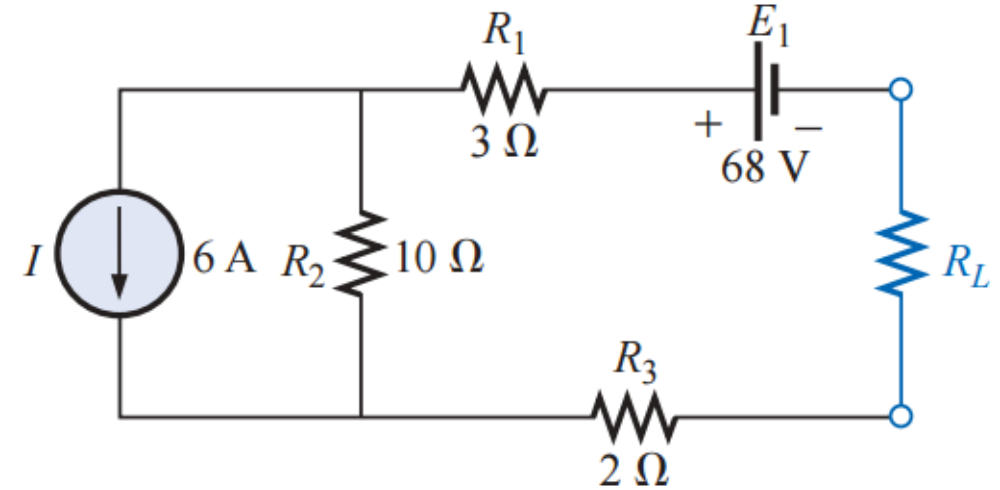



# Maximum Power Transfer Theorem

$$V_1 = V_3 = 0 \text{ V}$$

$$V_2 = I_2 R_2 = IR_2 = (6 \text{ A})(10 \Omega) = 60 \text{ V}$$

Applying Kirchhoff's voltage law,


$$\sum_{\odot} V = -V_2 - E_1 + E_{Th} = 0$$

and

$$E_{Th} = V_2 + E_1 = 60 \text{ V} + 68 \text{ V} = 128 \text{ V}$$

Thus,
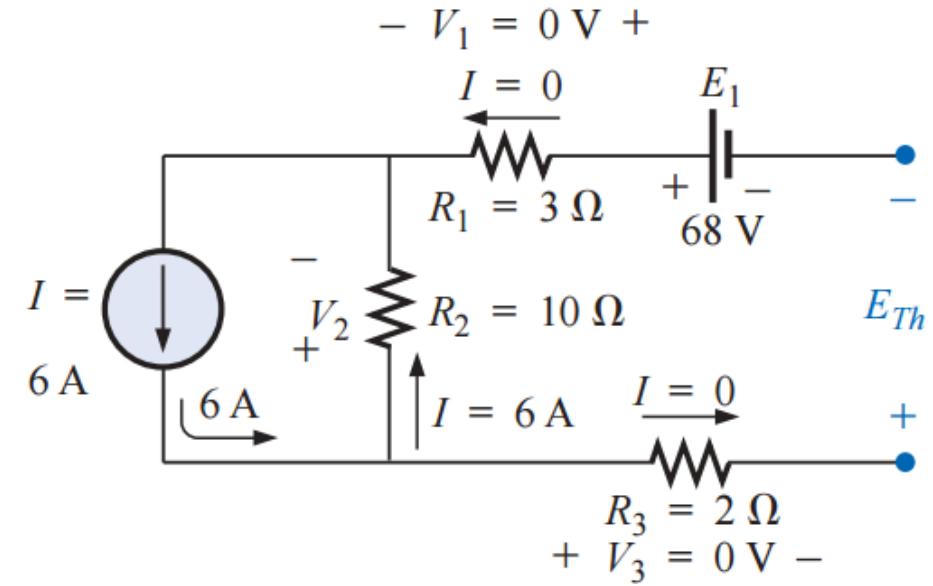
$$P_{L_{\max}} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(128 \text{ V})^2}{4(15 \Omega)} = \mathbf{273.07 \text{ W}}$$





# Maximum Power Transfer Theorem

**Example 3:** Find the value of  $R_L$  for maximum power in the figure below, then find the maximum power

**Solution:**

**Calculating the ( $R_{Th}$ ):**

$$R_{Th} = 2 + 3 + (6 \parallel 12) = 5 + \left(\frac{6 \times 12}{6 + 12}\right) = 9\Omega$$

**Calculating the ( $E_{Th}$ ):** Using Mesh

For loop 2:




$$I_2 = -2 \text{ A}$$

For loop 1

$$(6 + 12)I_1 - 12I_2 = 12$$

$$18I_1 - 12(-2) = 12 \Rightarrow 18I_1 + 24 = 12$$
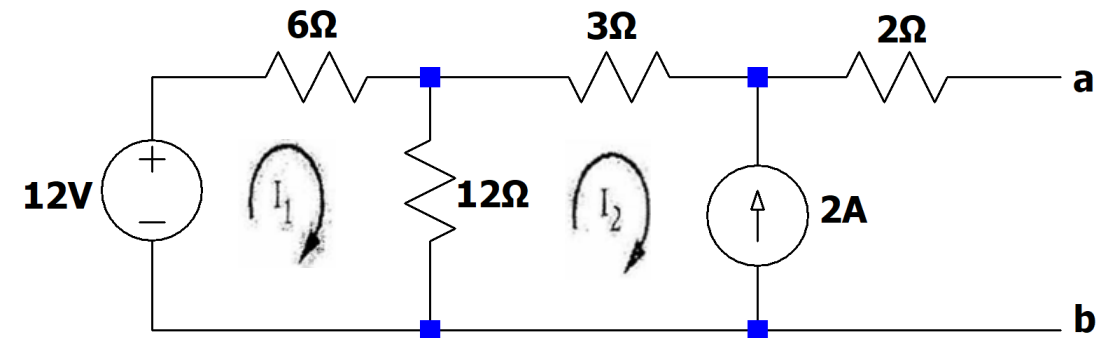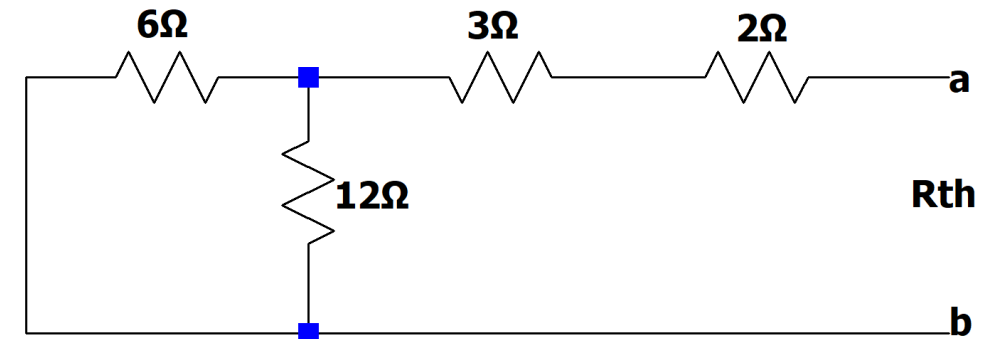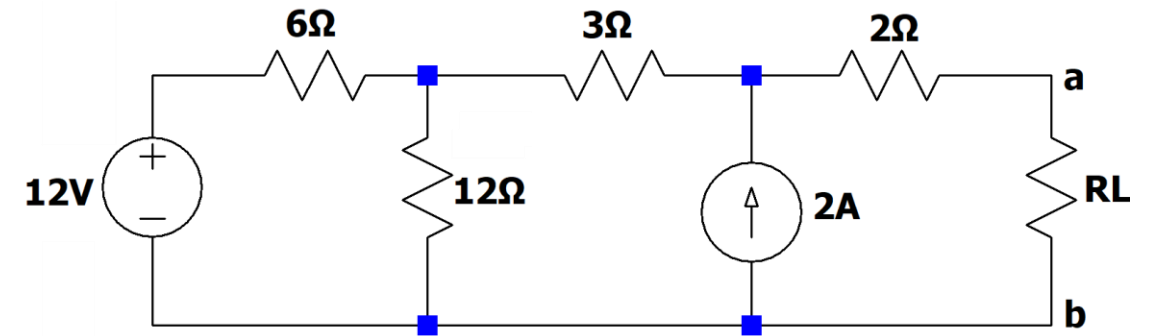
$$I_1 = \frac{-12}{18} = \frac{-2}{3} \text{ A}$$





# Maximum Power Transfer Theorem

Applying KVL around the other loop:

$$12 - 6I_1 - 3I_2 - 2(0) - E_{Th} = 0$$

$$12 - 6\left(\frac{-2}{3}\right) - 3(-2) = E_{Th}$$

$$E_{Th} = 22 \text{ V}$$

For maximum power transfer:

$$R_L = R_{Th} = 9\Omega$$

And maximum power is :

$$P_{max} = \frac{v_{Th}^2}{4R_{Th}}$$

$$P_{max} = \frac{22^2}{4 \times 9} = 13.44 \text{ W}$$

